

List of Experiments

1. Demonstrate the working of AND, OR, and NOT gates.
2. Demonstrate the working of NAND, NOR and XOR gates.
3. Design and implement the half-adder and demonstrate the working on simulator.
4. Design and implement the full-adder and demonstrate the working on simulator in two scenarios.
 - a. Using AND, OR and XOR gates
 - b. Using two half adder
5. Design 8-input multiplexors and demonstrate the working on simulator.
6. Design the circuit diagram for the following Boolean expression using 2-input gates.
$$\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$
 - a. Without simplification
 - b. With simplification
7. Demonstrate the working of S-R, J-K, T and D flip-flops.
8. Design and implements the 4-bit shift register in following scenarios.
 - a. Serial Input Serial Output
 - b. Serial Input Parallel Output
 - c. Parallel Input Serial Output
 - d. Parallel Input Parallel Output
9. Design and implement modulo 8 Synchronous counter using D flip-flops.
10. Design 3-bit ripple counter using J-K flip flops.

Resources To be Followed

Logisim Software: (<https://sourceforge.net/projects/circuit/>)

- 1) <https://www.youtube.com/watch?v=NAITQqdOw7c&list=PLvjlcTfwDj4spSN4g3S8IHbqY4Qkb5LxP>
- 2) https://www.youtube.com/watch?v=RdnT_Ujq72E&list=PL9Tu_yD7oJURQqPEAQ78FggiDeiK7MqVb
- 3) <https://www.youtube.com/watch?v=lvYCchzQTyE&list=PL7wffs-oJ6x3ey5kFlCe-qSaVsw4aHkYK>
- 4) https://www.youtube.com/watch?v=fh9uxAiqgow&list=PLc61Ym_C47gpcBlo5ZxGI5RDd-cx3gjal